

Cs211


Spring 2017

Lab 1

Using the procedure described in Master Tutorial Design:

- Half adder
- Full-adder using gates
- Full-adder using Half adder as a component
- 4 bit adder using 1bit Full adder as a component
- Verify all your designs in simulation
- Program the FPGA board and verify it works correctly.
- Write a detailed report following format given to you.


HALF-Adder

 


(a) The four possible cases

| $x \quad y$ | | Carry c | Sum s |
|-------------|---|--------------|------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

(b) Truth table

 


(c) Circuit

 


(d) Graphical symbol

Full Adder Circuit

 


(a) Block diagram

 

(b) Detailed diagram

An n -bit ripple-carry adder

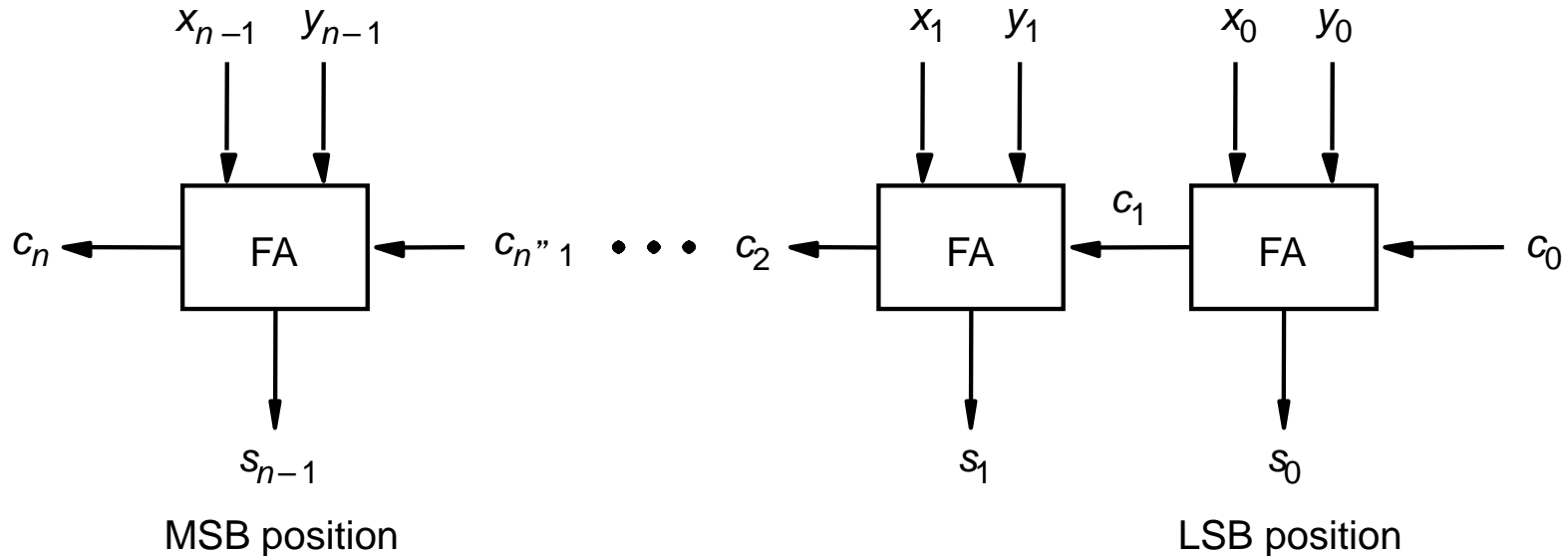

Denote by Δt time 1-Bit Full adder computes addition of two bits and carry.

Question: How much time it takes to compute the sum of two 32 bits words ?